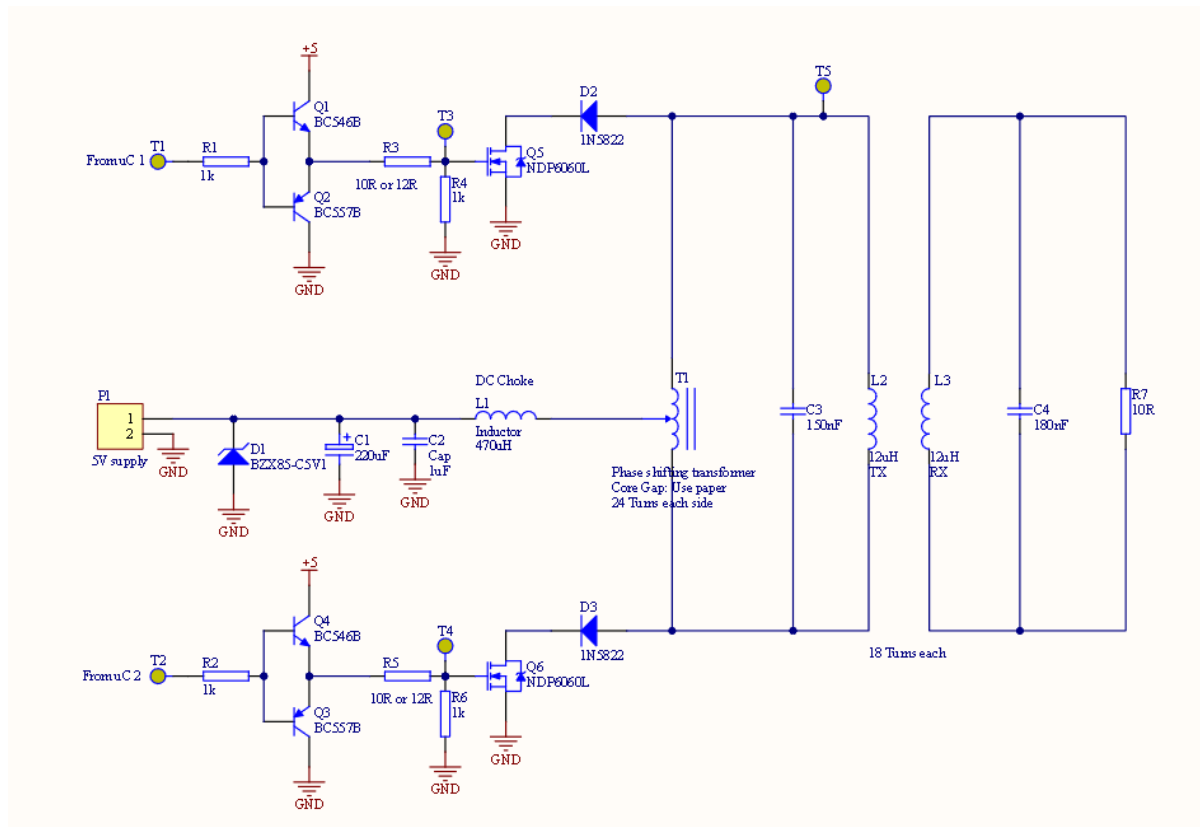


# Wireless Power Transfer Circuit Project





## Contents

|                                                 |   |
|-------------------------------------------------|---|
| Wireless Power Transfer Schematic .....         | 1 |
| Wireless Power Transfer Full Construction ..... | 2 |
| MCU Output Signals (T1 and T2) .....            | 2 |
| Channel 1 .....                                 | 3 |
| Channel 2 .....                                 | 3 |
| MOSFET Gate Signals (T3 and T4) .....           | 3 |
| Channel 1 .....                                 | 3 |
| Channel 2 .....                                 | 3 |
| Transmission and Receiving Signals (T5) .....   | 4 |
| Channel 1 .....                                 | 4 |
| Channel 2 .....                                 | 4 |
| Efficiency .....                                | 4 |
| Offload Current .....                           | 5 |


## Wireless Power Transfer Schematic


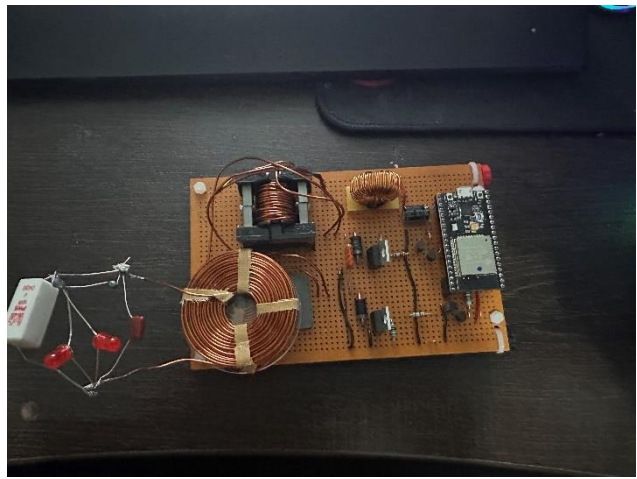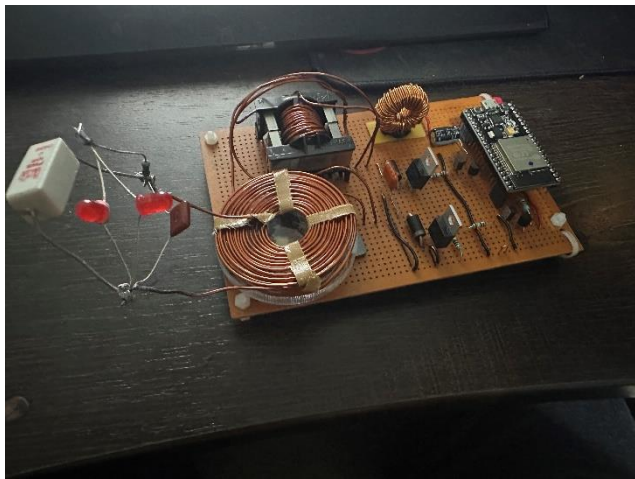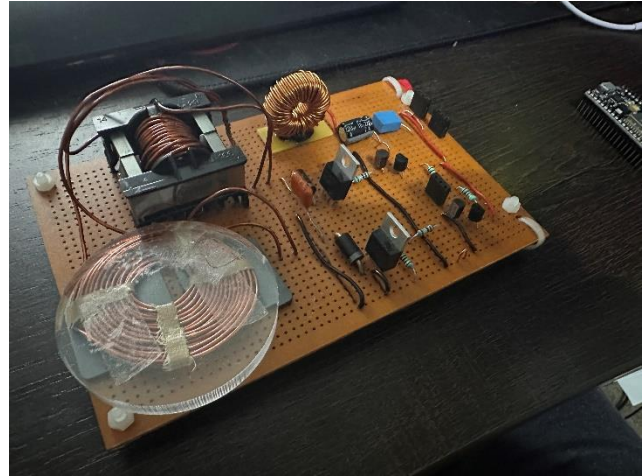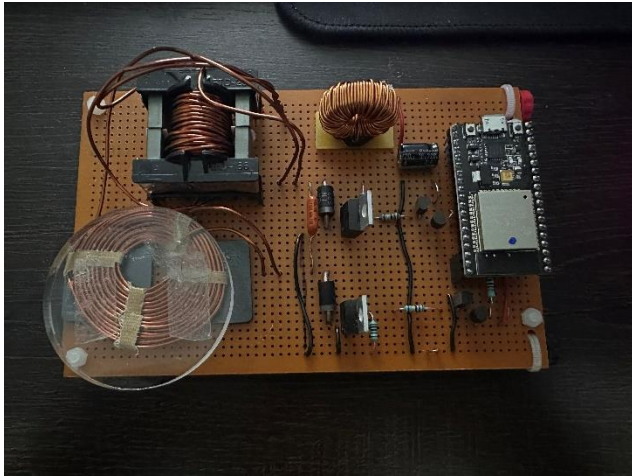
## Wireless Power Transfer Full Construction



## MCU Output Signals (T1 and T2)

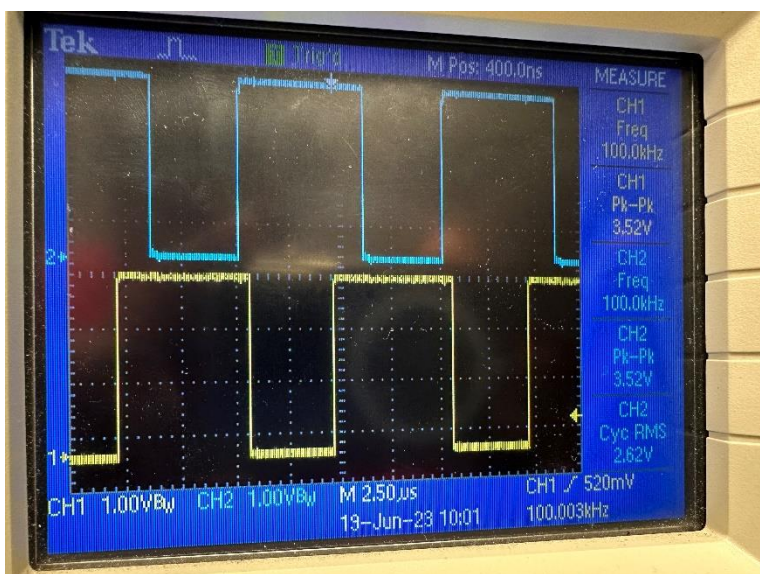

### Channel 1

Frequency: 100kHz

Amplitude: 3.56V

### Channel 2


Frequency: 100kHz

Amplitude: 3.52V

RMS: 2.63V

- Based on the waveforms, I have noticed there is no switching noise.
- Input voltage was 3.3V

## MOSFET Gate Signals (T3 and T4)

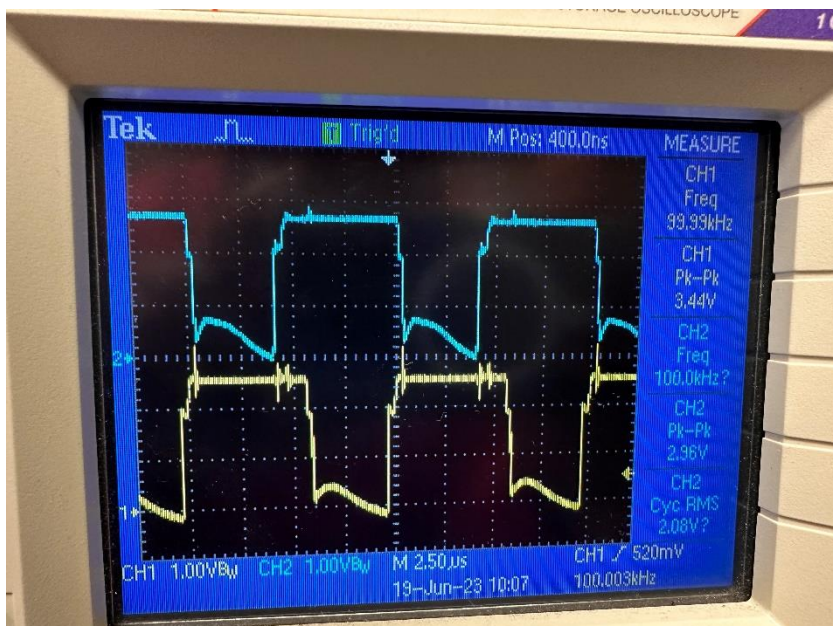

### Channel 1

Frequency: 99.99kHz

Amplitude: 3.44V

### Channel 2

Frequency: 100kHz


Amplitude: 2.96V

RMS: 2.08V



- Input voltage is 2.6V
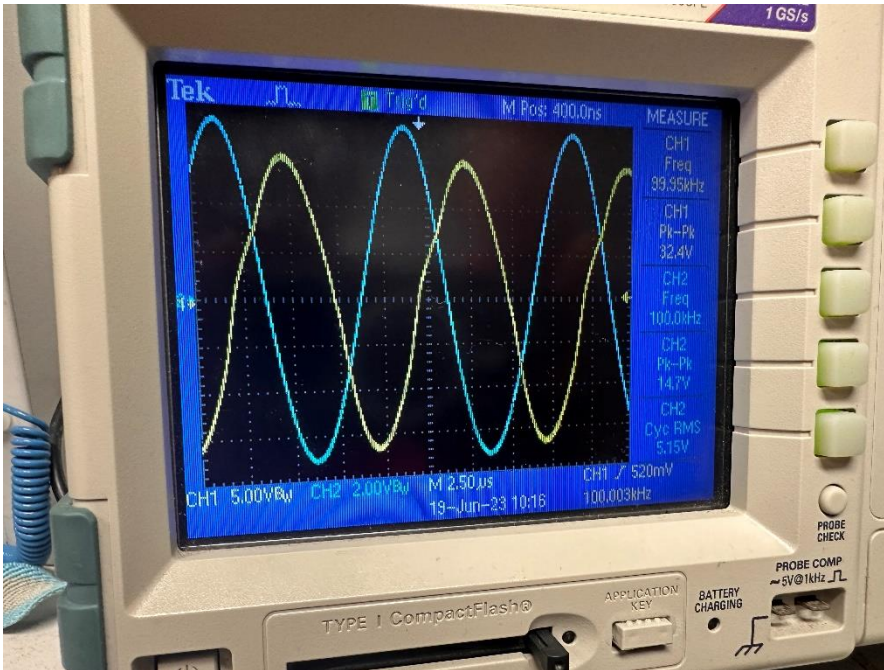
## Transmission and Receiving Signals (T5)



### Channel 1

Frequency: 99.95kHz

Amplitude: 32.4V

### Channel 2

Frequency: 100kHz

Amplitude: 14.7V

RMS: 5.15V



## Efficiency

Input Power (power when receiving coils are placed) = 4.88W

Output Power = 2.704 W

Efficiency % = Output Power / Input Power = 2.704 / 4.88 = 56.5%

## Offload Current

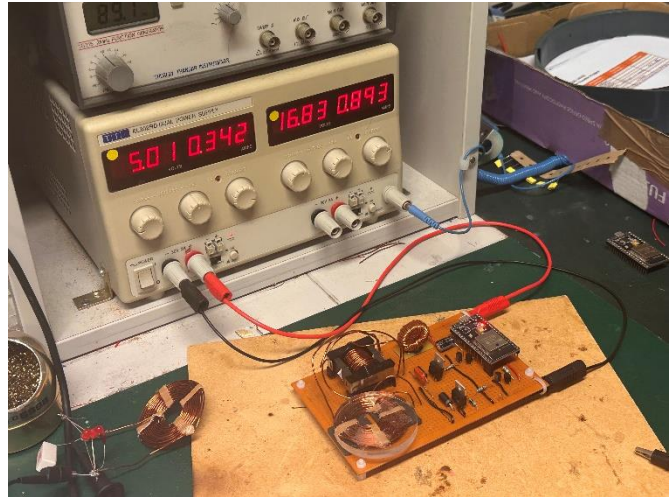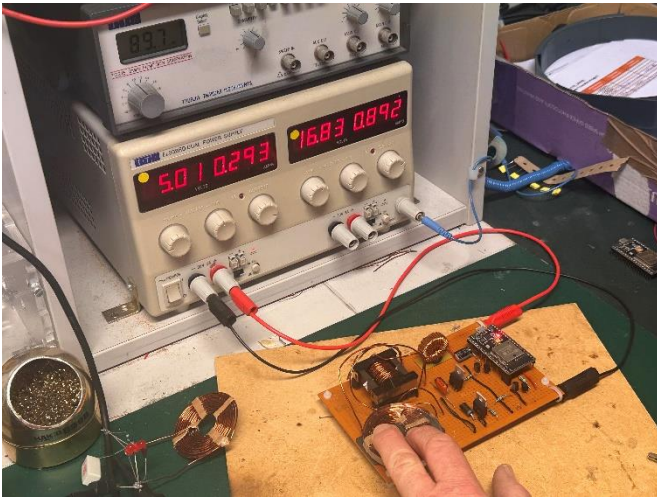

- Offload Current when pressing on coils is 0.293A
- Offload Current when coils are untouched is 0.342A

Because larger current levels would result in more current being lost during idleness, I was able to reach a low offload current, which is advantageous.